#### **VHDL CODE FOR 8-BIT SEQUENCE DETECTOR:**

```
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity FSM is
Port ( PATTERN : in STD_LOGIC_VECTOR(7 DOWNTO 0);
RST N: in STD LOGIC;
SDI: in STD LOGIC;
SCK: in STD LOGIC;
SEQ_DETECTED: out STD_LOGIC);
end FSM;
architecture FSM of FSM is
type state_type is(STATE_0, STATE_1, STATE_2, STATE_3, STATE_4, STATE_5, STATE_6,
STATE_7, STATE_8);
signal present_state: state_type;
signal next_state: state_type;
signal pattern_n: STD_LOGIC_Vector(7 downto 0);
begin
process (RST_N, SCK)
begin
       if (RST_N = '0') then
       present state <= STATE 0;
       elsif (rising_edge(SCK)) then
       present_state <= next_state;</pre>
       end if;
end process;
process(RST_N)
begin
       if(RST_N = '1' \text{ and } RST_N' \text{ event}) \text{ then}
       pattern_n <= pattern;</pre>
       end if;
end process;
process(present_state, SDI,pattern_n)
begin
next state <= present state;</pre>
SEQ_DETECTED <= '0';
case present state is
when STATE_0 => if(SDI = pattern_n(7)) then
                                      next_state <= STATE_1;</pre>
```


end if:

```
when STATE_1 = if(SDI = pattern_n(6)) then
                                 next_state <= STATE_2;</pre>
                                          elsif(SDI = pattern_n(7)) then
                                          next_state <= STATE_1;</pre>
                                          else
                                          next_state <= STATE_0;</pre>
                                          end if;
when STATE_2 \Rightarrow if(SDI = pattern_n(5)) then
                                          next_state <= STATE_3;</pre>
                                          elsif(SDI = pattern_n(7)) then
                                          next_state <= STATE_1;</pre>
                                          else
                                          next_state <= STATE_0;</pre>
                                          end if:
when STATE_3 => if(SDI = pattern_n(4)) then
                                          next_state <= STATE_4;</pre>
                                          elsif(SDI = pattern_n(7)) then
                                          next_state <= STATE_1;</pre>
                                          else
                                          next state <= STATE 0;
                                          end if;
when STATE 4 \Rightarrow if(SDI = pattern n(3)) then
                                          next_state <= STATE_5;</pre>
                                          elsif(SDI = pattern_n(7)) then
                                          next_state <= STATE_1;</pre>
                                          next_state <= STATE_0;</pre>
                                          end if:
when STATE_5 => if(SDI \le pattern_n(2)) then
                                          next_state <= STATE_6;</pre>
                                          elsif(SDI \le pattern_n(7)) then
                                          next_state <= STATE_1;</pre>
                                          else
                                          next_state <= STATE_0;</pre>
                                          end if;
when STATE_6 => if(SDI = pattern_n(1)) then
                                          next state <= STATE 7;</pre>
                                          elsif(SDI = pattern_n(7)) then
                                          next_state <= STATE_1;</pre>
                                          else
                                          next_state <= STATE_0;</pre>
when STATE_7 => if(SDI = pattern_n(0)) then
```

```
next_state <= STATE_8;
elsif (SDI = pattern_n(7)) then
next_state <= STATE_1;
else
next_state <= STATE_0;
end if;
when STATE_8 => if (SDI = pattern_n(7)) then
next_state <= STATE_1;
else next_state <= STATE_1;
else next_state <= STATE_0;
end if;

SEQ_DETECTED <= '1';
end case;
end process;
end FSM;</pre>
```

#### **BLOCK DIAGRAM:**

 


#### **DESCRIPTION:**

The basic function of this 8-bit sequence detector is to monitor the serial incoming data and assert the output flag signal when a certain sequence (data pattern) is detected. Here PATTERN LATCH has an input of 7 bit pattern whose operation is controlled by the RST\_N(Reset) signal. Thus if RST\_N is '1' or high, the 8 bit sequence will be detected and if RST\_N is '0' or low, system will be reset. SDI is the sequence detector input given which has controller signals, RST\_N and SCK(Clock). Here sequence will be detected only at the rising edge of the SCK and only when the RST\_N is high. A new data pattern will

only be detected at the rising edge of the RST\_N. When the pattern is detected the SEQ\_DETECTED signal will go high for one clock cycle showing that the sequence has been detected successfully.

 The Synthesis of the figure in Xilinx Simulator gives the following RTL Schematic showing the pattern Latch and Sequence detector.



#### **TEST BENCH:**

LIBRARY ieee;

USE ieee.std\_logic\_1164.ALL;

USE ieee.std\_logic\_unsigned.all;

USE ieee.numeric\_std.ALL;

ENTITY testbench\_vhd IS

END testbench\_vhd;

ARCHITECTURE behavior OF testbench\_vhd IS

```
-- Component Declaration for the Unit Under Test (UUT)
COMPONENT FSM
PORT(


PATTERN: IN std_logic_vector(7 downto 0);
RST_N: IN std_logic;
SDI: IN std_logic;
SCK: IN std_logic;
SEQ_DETECTED: OUT std_logic
);
```

```
END COMPONENT:
       --Inputs
       SIGNAL RST_N: std_logic := '0';
       SIGNAL SDI: std_logic := '0';
       SIGNAL SCK: std_logic := '0';
       SIGNAL PATTERN: std_logic_vector(7 downto 0) := (others=>'0');
       --Outputs
       SIGNAL SEQ_DETECTED: std_logic;
 --Variables
       SIGNAL seq_input:std_logic_vector(15 downto 0):="1110010101010100110";
BEGIN
       -- Instantiate the Unit Under Test (UUT)
       uut: FSM PORT MAP(
              PATTERN => PATTERN,
              RST_N => RST_N,
              SDI \Rightarrow SDI,
              SCK => SCK,
              SEQ DETECTED => SEQ DETECTED
       );
SCK <= not SCK after 1 ns;
       tb: PROCESS
 BEGIN
       wait until SCK'event and SCK = '1';
  wait until SCK'event and SCK = '1';
       wait until SCK'event and SCK = '1';
                             RST_N <= '1';
                             pattern <= "11111000";
              wait for 10 ns;
                             RST_N \le 0';
              wait for 80 ns;
                             RST_N \le '1';
                             pattern <="11100101";
              wait for 20 ns;
                             RST_N \le 1';
                             wait;
       END PROCESS;
 PROCESS
       BEGIN
              for i in 15 downto 0 loop
```


SDI <= seq\_input(i);
 wait until SCK'event and SCK='1';
 end loop;
END PROCESS;
END;</pre>
 
#### **RESULTS:**

In **case 1** Time =5 ns RST\_N becomes 1 Pattern changes to F8 i.e., '11111000' SEQ\_DETECTED signal is '0'



 
In case 2 Time =15 ns RST\_N becomes 0 Pattern changes to F8 i.e., '11111000' SEQ\_DETECTED signal is '0'



In **case 3** Time =95 ns RST N becomes 1

Pattern changes to E5 i.e., '11100011'

SEQ\_DETECTED signal is '0'

 


#### Case4

After 7 cycles the SEQ\_DETECTED signal becomes '1' after detecting the sequence pattern at 115 ns.



#### **GATE LEVEL SCHEMATIC:**

 

#### **GATE LEVEL NETLIST(Final.v):**

/\*

# Generated by: Cadence Encounter 10.13-s292\_1
# OS: Linux x86\_64(Host ID wks18.ecel.ufl.edu)

# Generated on: Thu Mar 20 17:34:46 2014

# Design: FSM

# Command: saveNetlist -excludeLeafCell final.v

```
*/
module FSM (
       PATTERN,
       RST_N,
       SDI,
       SCK,
       SEQ_DETECTED);
 input [7:0] PATTERN;
 input RST_N;
 input SDI;
 input SCK;
 output SEQ_DETECTED;
 // Internal wires
 wire n5;
 wire n6;
 wire n7;
 wire n8;
 wire n9;
 wire n10;
 wire n11;
 wire n12;
 wire n13;
 wire n14;
 wire n15;
 wire n16;
 wire n17;
 wire n18;
 wire n19;
 wire n20;
 wire n21;
 wire n22;
 wire n23;
 wire n24;
 wire n25;
 wire n26;
 wire n27;
 wire n28;
 wire n29;
 wire n30;
 wire n31;
 wire n32;
 wire n33;
 wire n34;
 wire n35;
 wire n36;
 wire n37;
 wire n38;
 wire n39;
 wire n40;
 wire n41;
```

```
wire n42;
wire n43;
wire n44;
wire n45;
wire n46:
wire n47;
wire n48;
wire n49;
wire n50;
wire n51;
wire n52:
wire n53;
wire n54;
wire n55;
wire n56;
wire n57;
wire [3:0] pr_state;
wire [7:0] pr_next;
DFFPOSX1 pr_next_reg_7_ (.Q(pr_next[7]),
     .D(PATTERN[7]),
     .CLK(RST_N));
DFFPOSX1 pr_next_reg_6_ (.Q(pr_next[6]),
     .D(PATTERN[6]),
     .CLK(RST N));
DFFPOSX1 pr_next_reg_5_ (.Q(pr_next[5]),
     .D(PATTERN[5]),
     .CLK(RST_N));
DFFPOSX1 pr_next_reg_4_ (.Q(pr_next[4]),
     .D(PATTERN[4]),
     .CLK(RST_N));
DFFPOSX1 pr_next_reg_3_ (.Q(pr_next[3]),
     .D(PATTERN[3]),
     .CLK(RST N));
DFFPOSX1 pr_next_reg_2_ (.Q(pr_next[2]),
     .D(PATTERN[2]),
     .CLK(RST_N));
DFFPOSX1 pr_next_reg_1_ (.Q(pr_next[1]),
     .D(PATTERN[1]),
     .CLK(RST_N));
DFFPOSX1 pr_next_reg_0_ (.Q(pr_next[0]),
     .D(PATTERN[0]),
     .CLK(RST_N));
DFFSR pr_state_reg_3_ (.S(1'b1),
     .R(RST_N),
     .Q(pr_state[3]),
     .D(n54),
     .CLK(SCK));
DFFSR pr_state_reg_1_ (.S(1'b1),
     .R(RST_N),
     .Q(pr_state[1]),
```


```
.D(n56),
     .CLK(SCK));
DFFSR pr_state_reg_0_ (.S(1'b1),
     .R(RST N),
     .Q(pr state[0]),
     .D(n57),
     .CLK(SCK));
DFFSR pr_state_reg_2_(.S(1'b1),
     .R(RST_N),
     .Q(pr_state[2]),
     .D(n55),
     .CLK(SCK));
OR2X2 U7 (.Y(n17),
     .B(n10),
     .A(n18));
OR2X2 U8 (.Y(n39),
     .B(pr_next[2]),
     .A(n15));
INVX2 U9 (.Y(n5),
     .A(n29));
INVX2 U10 (.Y(n6),
      .A(n46));
INVX2 U11 (.Y(n7),
     .A(n49));
INVX2 U12 (.Y(n8),
      .A(n16));
INVX2 U13 (.Y(n9),
     .A(pr_state[3]));
INVX2 U14 (.Y(n10),
     .A(pr_state[2]));
INVX2 U15 (.Y(n11),
      .A(n45));
INVX2 U16 (.Y(n12),
      .A(pr state[1]));
INVX2 U17 (.Y(n13),
      .A(pr_state[0]));
INVX2 U18 (.Y(n14),
     .A(n43));
INVX2 U19 (.Y(n15),
     .A(SDI));
NOR2X1 U20 (.Y(n54),
     .B(n17),
     .A(n16));
NAND3X1 U21 (.Y(n55),
     .C(n21),
     .B(n20),
     .A(n19));
NAND3X1 U22 (.Y(n20),
     .C(n22),
     .B(n10),
     .A(n8));
```

```
NAND3X1 U23 (.Y(n19),
      .C(n25),
      .B(n24),
      .A(n23));
NOR2X1 U24 (.Y(n25),
      .B(n10),
      .A(pr_state[3]));
OAI21X1 U25 (.Y(n56),
      .C(n21),
      .B(n27),
      .A(n26));
AOI21X1 U26 (.Y(n21),
      .C(n5),
      .B(n7),
      .A(n28));
OAI21X1 U27 (.Y(n29),
      .C(n6),
      .B(n15),
      .A(pr_next[2]));
NAND2X1 U28 (.Y(n27),
      .B(n9),
      .A(n10));
AOI22X1 U29 (.Y(n26),
      .D(n33),
      .C(n32),
      .B(n31),
      .A(n30));
NOR2X1 U30 (.Y(n32),
      .B(n13),
      .A(pr_state[1]));
NOR2X1 U31 (.Y(n30),
      .B(n12),
      .A(pr_state[0]));
AOI22X1 U32 (.Y(n57),
      .D(n36),
      .C(n35),
      .B(n24),
     .A(n34));
AOI21X1 U33 (.Y(n36),
      .C(n38),
      .B(n37),
      .A(n14));
OAI21X1 U34 (.Y(n38),
      .C(n41),
      .B(n40),
      .A(n39));
NAND3X1 U35 (.Y(n41),
      .C(n42),
      .B(n9),
      .A(n10));
OAI21X1 U36 (.Y(n42),
```


```
.C(n44),
      .B(n43),
      .A(n11));
OAI21X1 U37 (.Y(n44),
      .C(n13),
      .B(n31),
      .A(n14));
XOR2X1 U38 (.Y(n31),
      .B(pr_next[5]),
      .A(n15));
OAI22X1 U39 (.Y(n45),
      .D(pr_state[1]),
      .C(n33),
      .B(n22),
      .A(n12));
XOR2X1 U40 (.Y(n33),
      .B(pr_next[6]),
      .A(n15));
XOR2X1 U41 (.Y(n22),
      .B(pr_next[4]),
      .A(n15));
NAND2X1 U42 (.Y(n40),
      .B(n6),
      .A(pr next[7]);
NAND3X1 U43 (.Y(n46),
      .C(n47),
      .B(pr_state[2]),
      .A(pr_state[0]));
NOR2X1 U44 (.Y(n47),
      .B(pr_state[1]),
      .A(pr_state[3]));
OAI21X1 U45 (.Y(n37),
      .C(n49),
      .B(n48),
      .A(n16));
NAND2X1 U46 (.Y(n48),
      .B(pr_state[2]),
     .A(n18));
XNOR2X1 U47 (.Y(n18),
      .B(pr_next[0]),
      .A(n15));
NAND3X1 U48 (.Y(n16),
      .C(pr_state[1]),
      .B(n9),
      .A(pr_state[0]));
AOI22X1 U49 (.Y(n35),
      .D(n28),
      .C(n7),
      .B(n50),
      .A(n24));
XOR2X1 U50 (.Y(n28),
```

```
.B(pr_next[1]),
       .A(n15));
 NAND3X1 U51 (.Y(n49),
       .C(n51),
       .B(pr_state[2]),
       .A(pr_state[1]));
 NOR2X1 U52 (.Y(n51),
       .B(pr_state[0]),
       .A(pr_state[3]));
 NAND2X1 U53 (.Y(n50),
       .B(n52),
       .A(pr_state[2]));
 OAI21X1 U54 (.Y(n52),
       .C(n9),
       .B(n23),
       .A(n14));
 XOR2X1 U55 (.Y(n23),
       .B(pr_next[3]),
       .A(n15));
 NOR2X1 U56 (.Y(n34),
       .B(n14),
       .A(pr_state[2]));
 XOR2X1 U57 (.Y(n43),
       .B(SDI),
       .A(pr_next[7]));
 NOR2X1 U58 (.Y(SEQ_DETECTED),
       .B(n53),
       .A(n9));
 NAND2X1 U59 (.Y(n53),
       .B(n10),
       .A(n24));
 NOR2X1 U60 (.Y(n24),
       .B(pr_state[1]),
       .A(pr_state[0]));
endmodule
```


#### LAYOUT:

 


#### **DRC CLEAN REPORT:**

 

#### LVS REPORT:

 



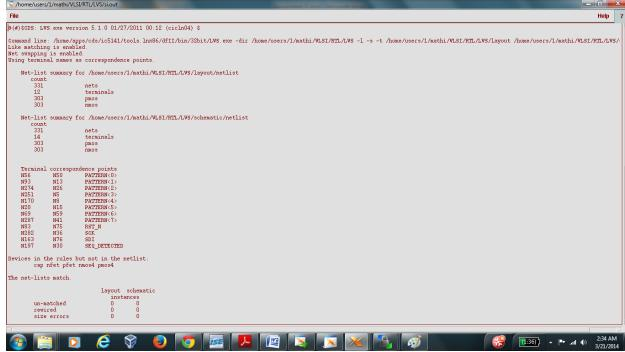

#### SI.OUT FILE:

@(#)\$CDS: LVS.exe version 5.1.0 01/27/2011 00:12 (cicln04) \$

Command line: /home/apps/cds/ic5141/tools.lnx86/dfII/bin/32bit/LVS.exe -dir /home/users/1/mathi/VLSI/PAR/LVS -l -s -t /home/users/1/mathi/VLSI/PAR/LVS/layout /home/users/1/mathi/VLSI/PAR/LVS/schematic

Like matching is enabled.

Net swapping is enabled.

Using terminal names as correspondence points.

Net-list summary for /home/users/1/mathi/VLSI/PAR/LVS/layout/netlist count

| 331 | nets      |
|-----|-----------|
| 0   | terminals |
| 303 | pmos      |
| 303 | nmos      |

Net-list summary for /home/users/1/mathi/VLSI/PAR/LVS/schematic/netlist

| count |           |
|-------|-----------|
| 331   | nets      |
| 14    | terminals |
| 303   | pmos      |
| 303   | nmos      |

Devices in the rules but not in the netlist: cap nfet pfet nmos4 pmos4

The net-lists match.

|                | layout schematic |           |  |
|----------------|------------------|-----------|--|
|                | instan           | instances |  |
| un-matched     | 0                | 0         |  |
| rewired        | 0                | 0         |  |
| size errors    | 0                | 0         |  |
| pruned         | 0                | 0         |  |
| active         | 606              | 606       |  |
| total          | 606              | 606       |  |
|                |                  |           |  |
|                | nets             |           |  |
| un-matched     | 0                | 0         |  |
| merged         | 0                | 0         |  |
| pruned         | 0                | 0         |  |
| active         | 331              | 331       |  |
| total          | 331              | 331       |  |
|                |                  |           |  |
|                | termir           | terminals |  |
| un-matched     | 0                | 0         |  |
| matched but    |                  |           |  |
| different type | 0                | 0         |  |
| total          | 0                | 14        |  |
|                |                  |           |  |

Probe files from /home/users/1/mathi/VLSI/PAR/LVS/schematic

| 1 1000 mes from / nome/ asers/ 1/ matm/ * ESI/1 my E * S/seneman |
|--|
| devbad.out:  |
| netbad.out:  |
| mergenet.out:  |
| termbad.out:   |
| prunenet.out:  |
| prunedev.out:  |
| audit.out:   |

| devbad.out:   |  |  |
|---------------|--|--|
| netbad.out:   |  |  |
| mergenet.out: |  |  |
| termbad.out:  |  |  |
| prunenet.out: |  |  |
| prunedev.out: |  |  |
| audit.out:    |  |  |

 $Probe\ files\ from\ /home/users/1/mathi/VLSI/PAR/LVS/layout$